

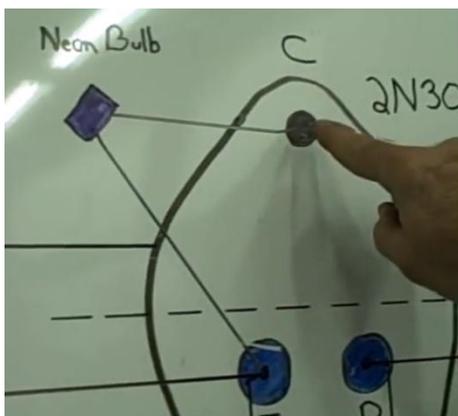
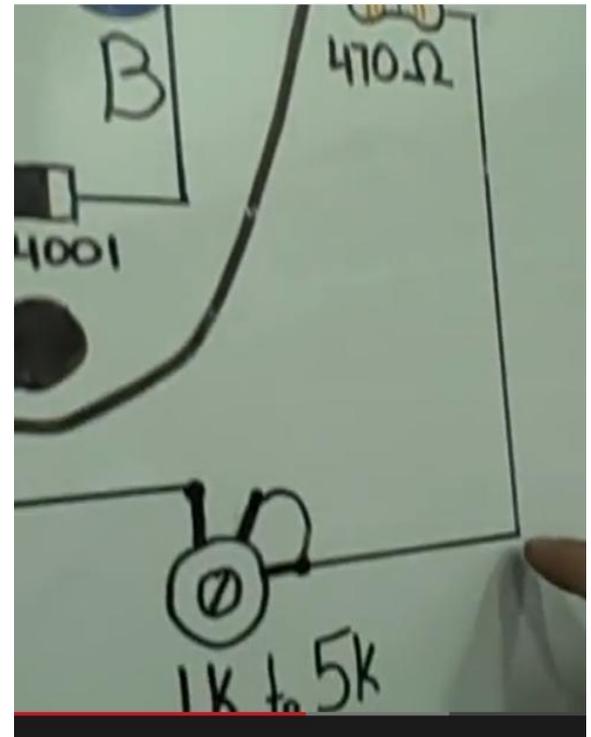
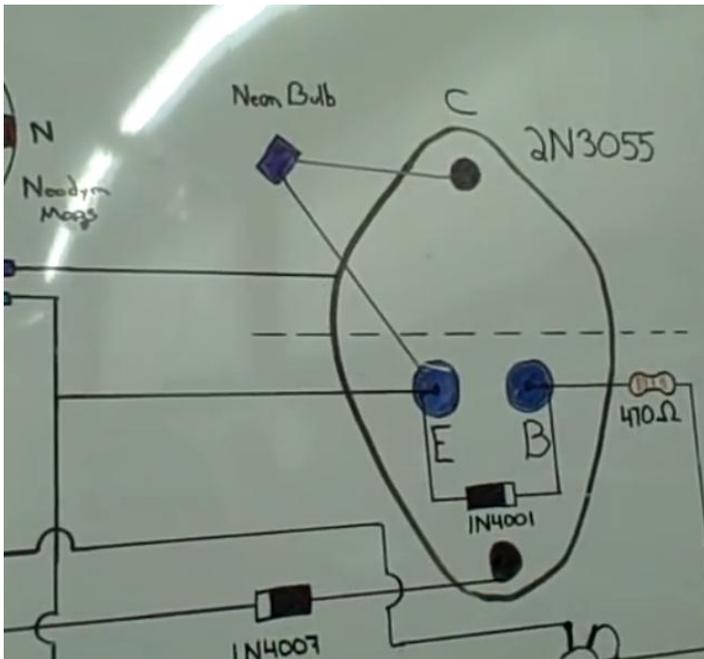
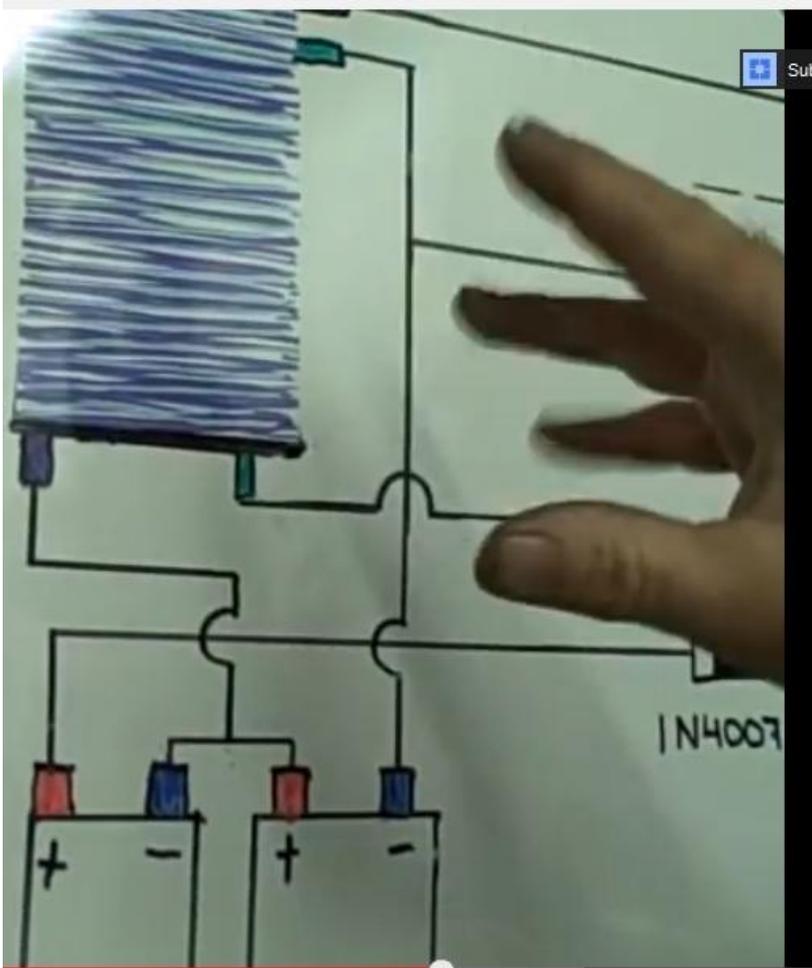



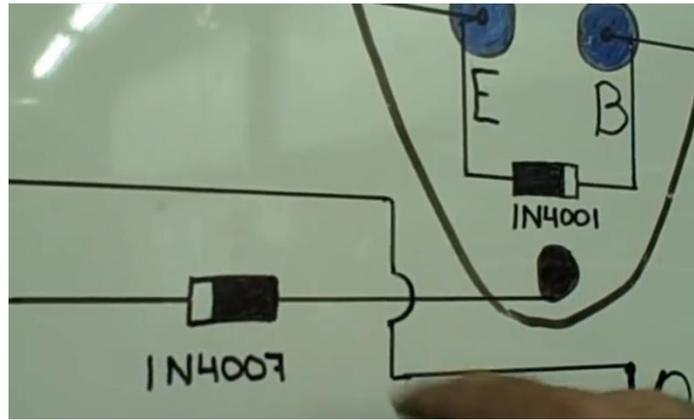
## Free Energy Technology


there are 2 bifilar coils placed in front of a rotating wheel with 4 magnets spaced 45 degrees apart from each other (the magnets are positioned so the north pole is facing outwards - the gap between the magnets and coil is one quarter inch -

The transistors are connected to each bifilar coil (the coils contain 2 gauges of wire) - there is a potmeter to govern speed - 2 lead acid (not lithium) batteries - 1 being a charging battery, the other for power output - 2n3055 transistor - connections - turn the transistor upside down so the connectors are lower or on the lower base of the back of the transistor - the one on the left is emitter and the one on the right is the base - the outer shell is known as the "collector" - The diode used 1n4001 is placed between the connector points of the base and emitter with the upper white part of the diode facing the base of the transistor - this allows the current of the diode to flow from emitter to base when the white strip is facing base - a 470 ohm resistor is then connected to the base of the transistor - this is then soldered to a 1 to 5 k potmeter - next a neon bulb is connected from the collector of the transistor to the emitter prong of the transistor - the neon bulb acts as a "draw away" current to prevent the transistor from overheating, or you may try a small motor or similar load to a neon bulb that gives visual as to how much current flow is occurring - from the emitter transistor, another wire goes to the 1st coil, - a diode called 1n4007 with the white strip facing away from the transistor and is attached to the collector base of the transistor - 1n4007 connects to the positive terminal of the charging battery - the charging battery and the power draw battery are both linked together via a positive and negative connection via a wire - which then connects to the larger wire in the bifilar coil - the larger size wire exiting out of the bifilar coil, is then connected to the collector base of the transistor - the smaller wire from the bifilar coil (24 gauge) is split into 2 areas one goes to the emitter of the transistor and the output of the smaller gauge wire connects to the negative on the primary battery - remember the other wire of the smaller gauge wire connects to the other end of the potmeter - the coil uses the following 2 gauge wires and turns - 900 turns of 20 gauge and 24 gauge wire - in the center of the coil is iron or iron ferrite rod -



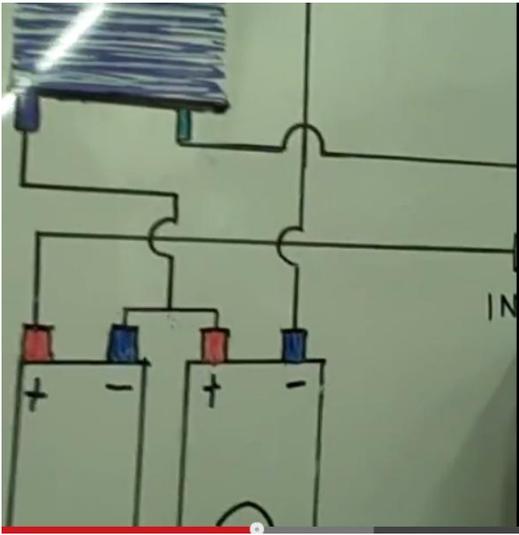

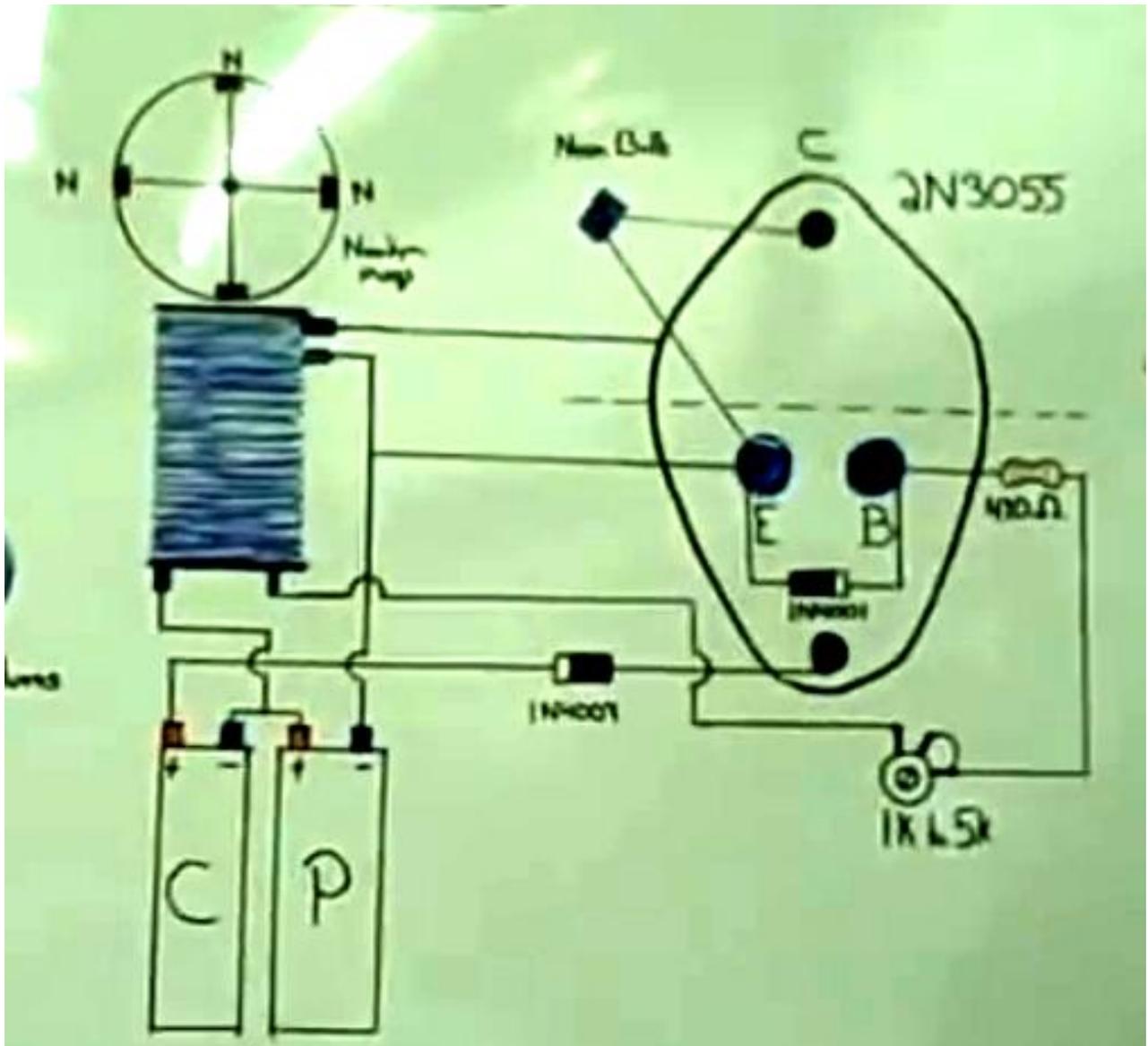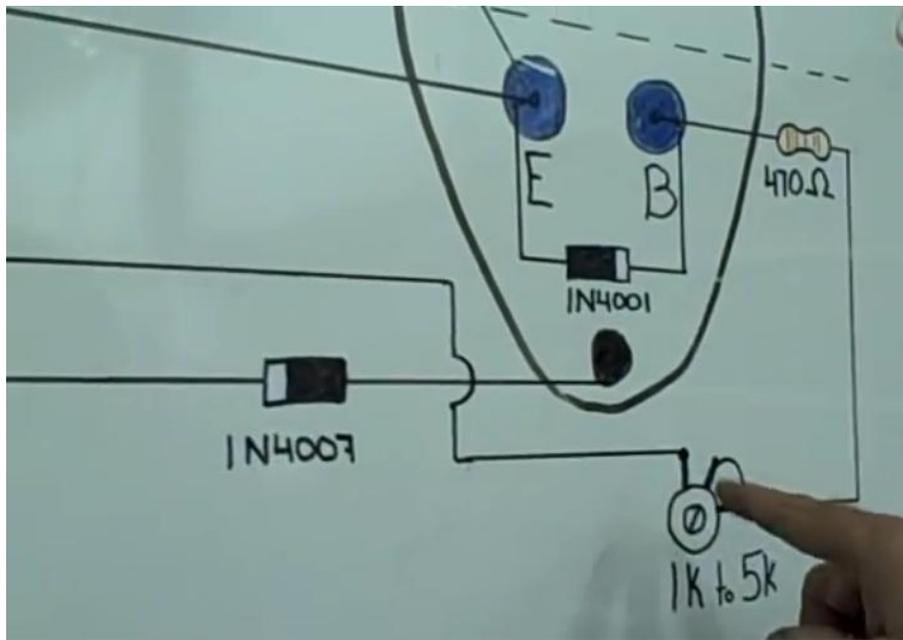

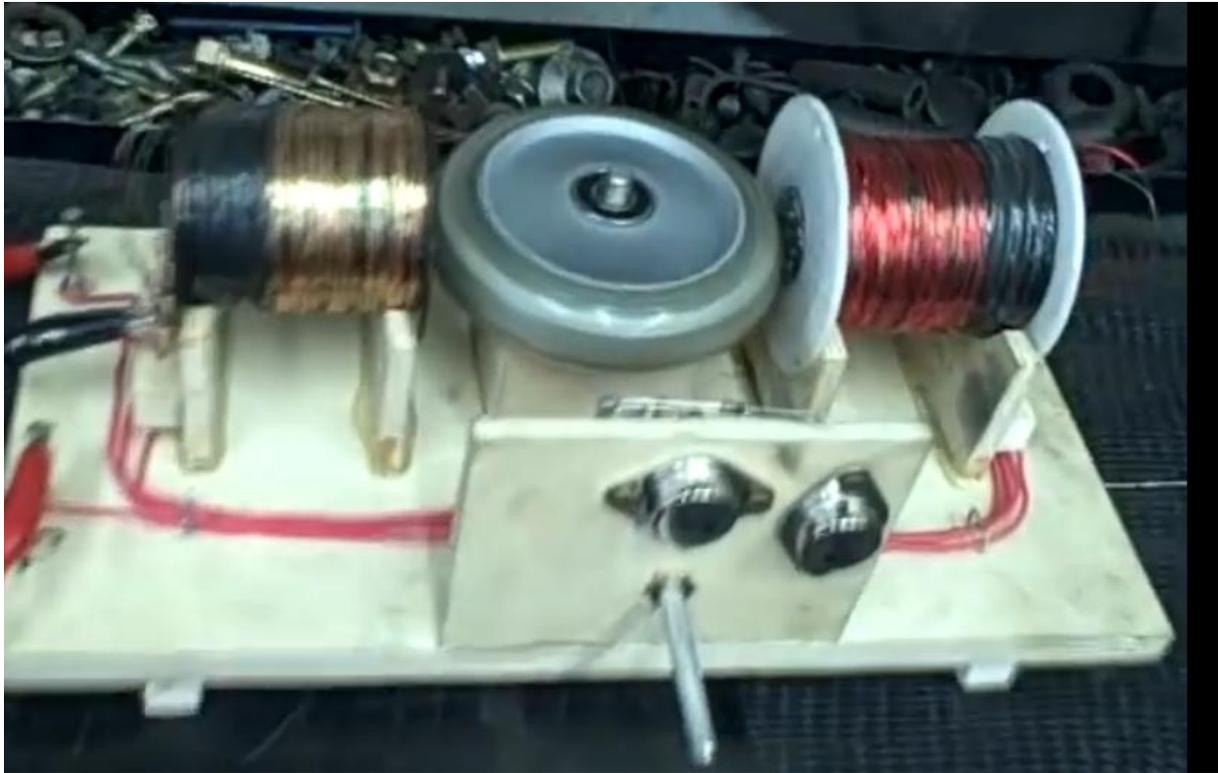

The diagram shows 1 coil connection for simplicity, to connect the 2<sup>nd</sup> coil, just follow the same path wiring as the first.